

## ASVAB-SECTION-5<sup>Q&As</sup>

ASVAB Section Five: Electronic Information

# Pass ASVAB ASVAB-SECTION-5 Exam with 100% Guarantee

Free Download Real Questions & Answers PDF and VCE file from:

https://www.geekcert.com/asvab-section-5.html

100% Passing Guarantee 100% Money Back Assurance

Following Questions and Answers are all new published by ASVAB
Official Exam Center

- Instant Download After Purchase
- 100% Money Back Guarantee
- 365 Days Free Update
- 800,000+ Satisfied Customers






### https://www.geekcert.com/asvab-section-5.html 2024 Latest geekcert ASVAB-SECTION-5 PDF and VCE dumps Download

QUESTION 1	
Voltage is also known as	
A. electrical potential	
B. current charge	
C. shock factor	
D. electronic strength	
Correct Answer: A	

#### **QUESTION 2**



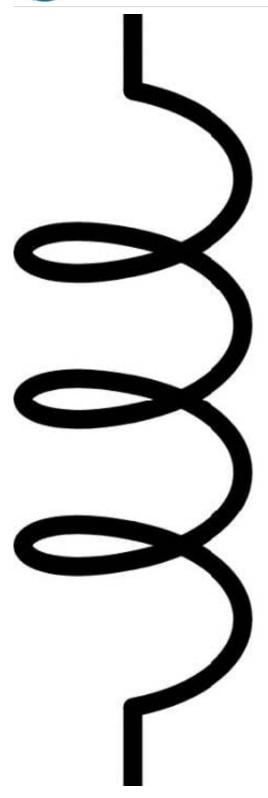

This symbol is the symbol for which of these electrical circuit components?

A. inductor

B. elevator

C. conductor




https://www.geekcert.com/asvab-section-5.html 2024 Latest geekcert ASVAB-SECTION-5 PDF and VCE dumps Download

D. resistor
Correct Answer: A
QUESTION 3
Induction is measured in
A. Henries
B. ohms
C. Franks
D. joules
Correct Answer: A
QUESTION 4
Two 8-ohm speakers are connected in parallel to an amplifier with a 24-volt output. What is the voltage across each speaker?
A. 6 volts
B. 12 volts
C. 18 volts
D. 24 volts
Correct Answer: D
Resistances in parallel have the same voltage across them.

#### **QUESTION 5**
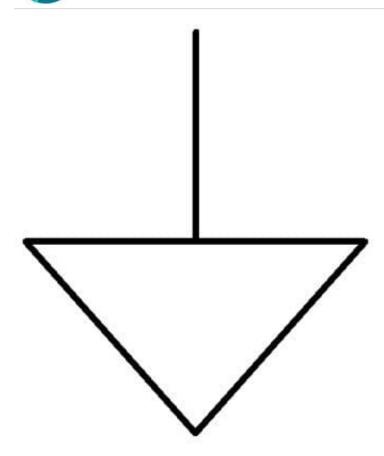
#### https://www.geekcert.com/asvab-section-5.html 2024 Latest geekcert ASVAB-SECTION-5 PDF and VCE dumps Download



The symbol in this diagram is the symbol for \_\_\_\_\_\_.

- A. lightning
- B. Earth ground
- C. power source
- D. signal ground

Correct Answer: D

ASVAB-SECTION-5
Practice Test

ASVAB-SECTION-5 Exam

Questions

ASVAB-SECTION-5
Braindumps